

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ


## Single-Stage Integrated Circuit Amplifier (Part 2)

- Common-Source Amplifier : High Frequency Response!




## Common-Source Amplifier : High Frequency Response

- The circuit is:

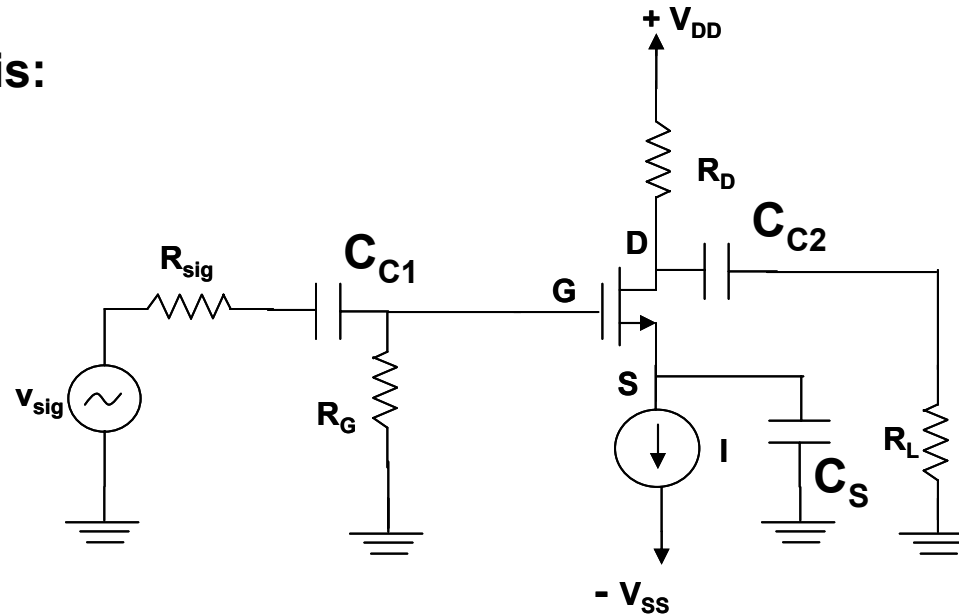


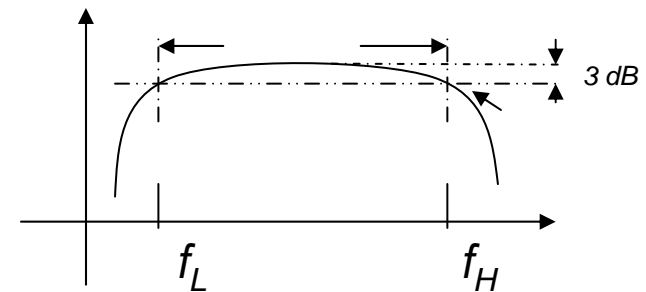- The MOSFET is replaced by its high-frequency model to determine the gain or the transfer function at  $f_H$ .
- At these frequencies (high)  $C_{C1}$ ,  $C_{C2}$ , and  $C_S$  will be behaving as perfect short circuits.
- ..contd.




## Common-Source Amplifier : High Frequency Response...contd

- So the circuit becomes:

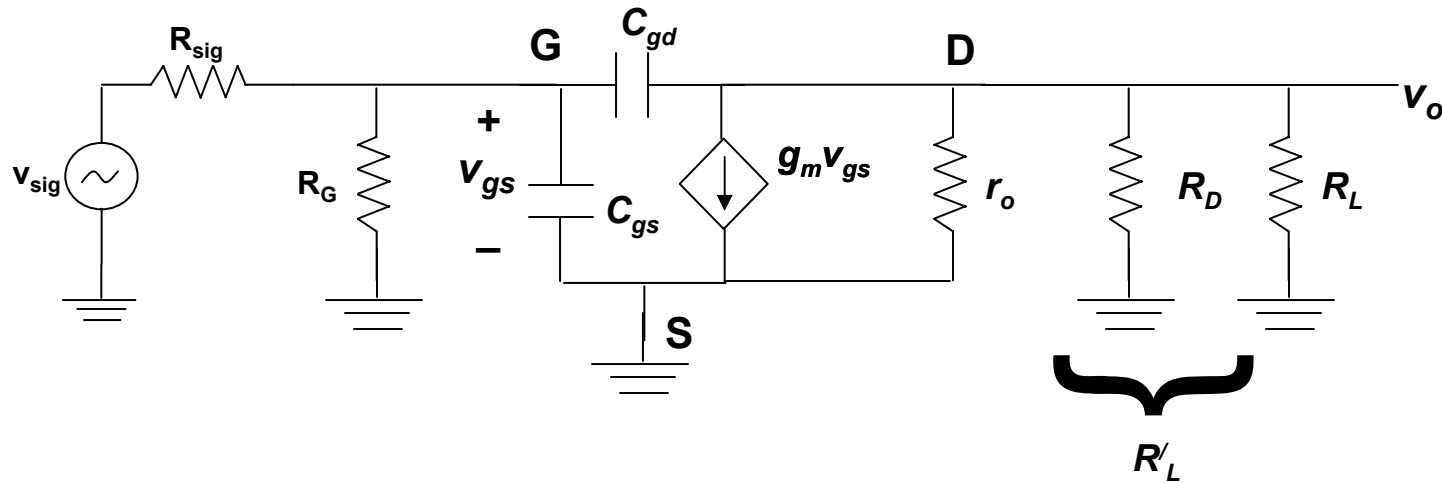

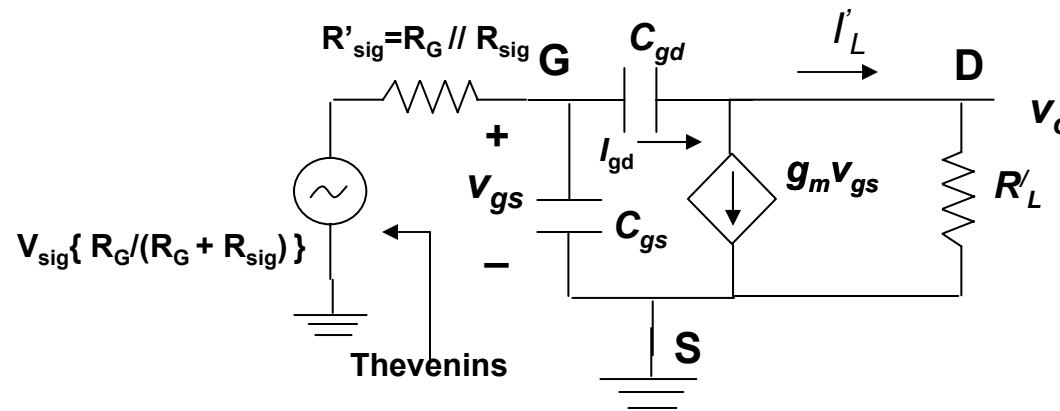- To deal with the bridging capacitor  $C_{gd}$  consider the following circuit:






## Common-Source Amplifier : High Frequency Response...contd

5

- So KCL at o/p node is:  $I_{gd} = g_m V_{gs} + I'_L$
- Or  $I'_L = I_{gd} - g_m V_{gs}$
- At and near  $f_H$   $I_{gd} \ll g_m V_{gs}$
- So  $I'_L = -g_m V_{gs}$
- And  $v_o = -g_m V_{gs} R'_L$

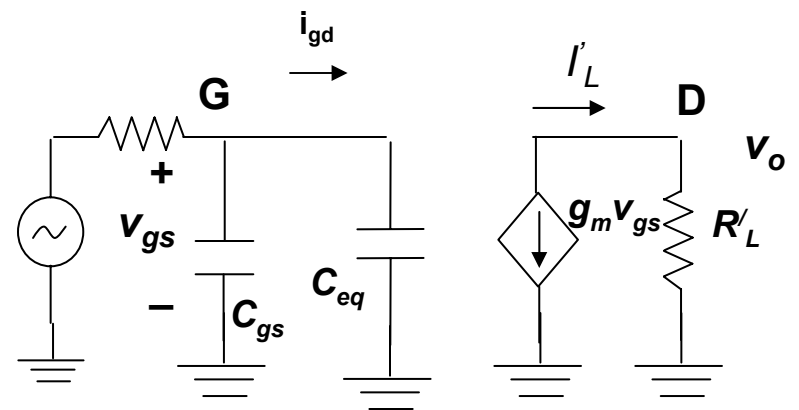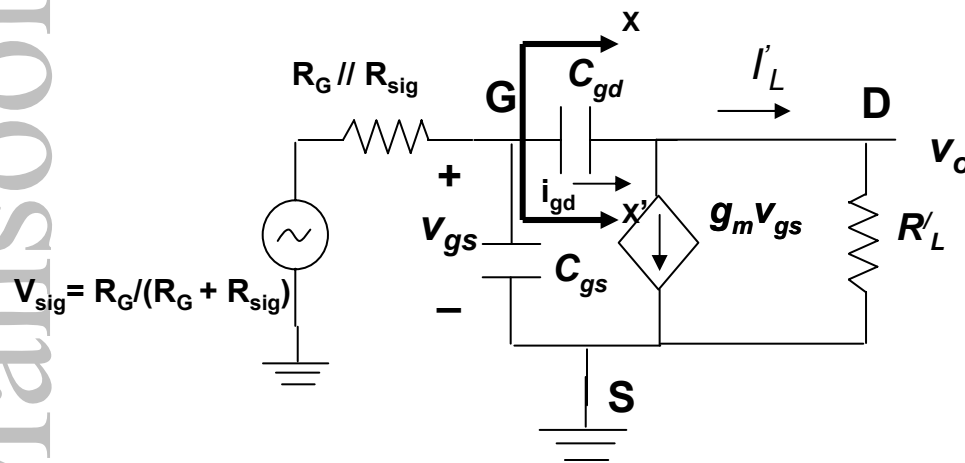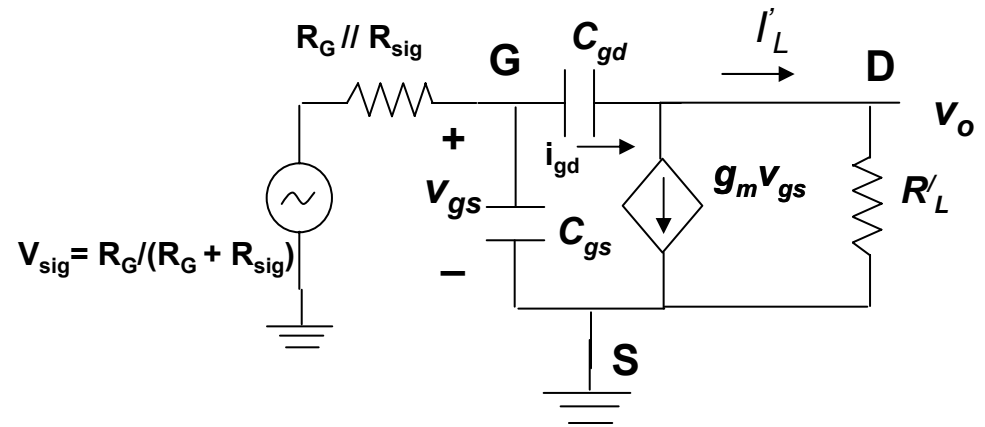- Because  $I = sCV$
- So  $I_{gd} = sC_{gd} (v_{gs} - v_o)$
- Or  $I_{gd} = sC_{gd} (v_{gs} - (-g_m V_{gs} R'_L))$
- And  $I_{gd} = sC_{gd} (1 + g_m R'_L) V_{gs}$
- Now consider:



## Common-Source Amplifier : High Frequency Response...contd

6

- Now  $I_{gd} = sC_{gd} (1 + g_m R'_L) V_{gs} = sC_{eq} V_{gs}$

- Which means  $C_{eq} = C_{gd} (1 + g_m R'_L)$

- So output voltage across  $C_{gs}$  :

$$v_{gs} = \left( \frac{R_G}{R_G + R_{sig}} v_{sig} \right) T_F$$


And :  $T_F = \frac{v_o}{v_i} = \left( \frac{1}{1 + \frac{s}{\omega_o}} \right)$  where  $\omega_o = 1/C_{in} R'_{sig}$   
3 dB or corner freq

- Hence:

$$v_{gs} = \left( \frac{R_G}{R_G + R_{sig}} v_{sig} \right) \left( \frac{1}{1 + \frac{s}{\omega_o}} \right)$$

Here  $C_{in} = C_{gs} + C_{eq} = C_{gs} + C_{gd} (1 + g_m R'_L)$

And  $R'_{sig} = R_{sig} // R_G$

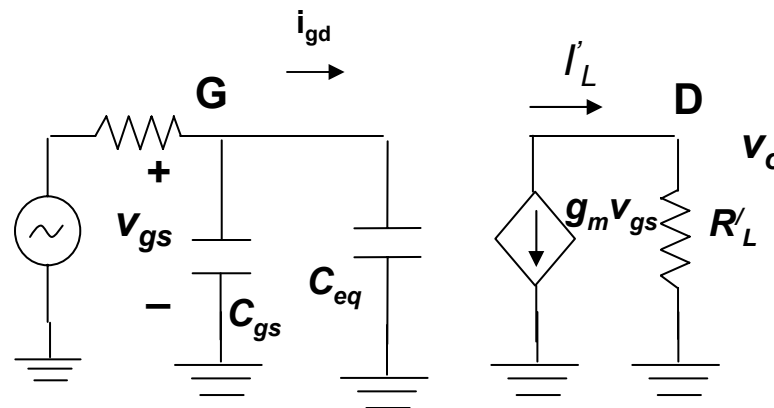

- ...contd!



## Common-Source Amplifier : High Frequency Response...contd

- Hence with: 
$$v_{gs} = \left( \frac{R_G}{R_G + R_{sig}} v_{sig} \right) \left( \frac{1}{1 + \frac{s}{\omega_o}} \right)$$

- We know  $v_o = -g_m v_{gs} R'_L$  or  $v_{gs} = -v_o / g_m R'_L$

- So  $v_{gs} = -v_o / g_m R'_L = \left( \frac{R_G}{R_G + R_{sig}} v_{sig} \right) \left( \frac{1}{1 + \frac{s}{\omega_o}} \right)$

- So hi-freq gain of CS amplifier:

$$\frac{v_o}{v_{sig}} = - \left( \frac{R_G}{R_G + R_{sig}} \right) g_m R'_L \left( \frac{1}{1 + \frac{s}{\omega_o}} \right)$$

Or: 
$$\frac{v_o}{v_{sig}} = \left( \frac{A_M}{1 + \frac{s}{\omega_H}} \right) \quad \text{where: } A_M = - \left( \frac{R_G}{R_G + R_{sig}} \right) g_m R'_L \quad \text{And: } f_H = \left( \frac{1}{2\pi C_{in} R'_{sig}} \right)$$


- Notice that in the expression for  $C_{eq} = C_{gd} (1 + g_m R'_L)$ , the factor  $(1 + g_m R'_L)$  is known as Miller multiplier and multiplication of  $C_{gd}$  by  $(1 + g_m R'_L)$  is known as Miller effect.

- Example!


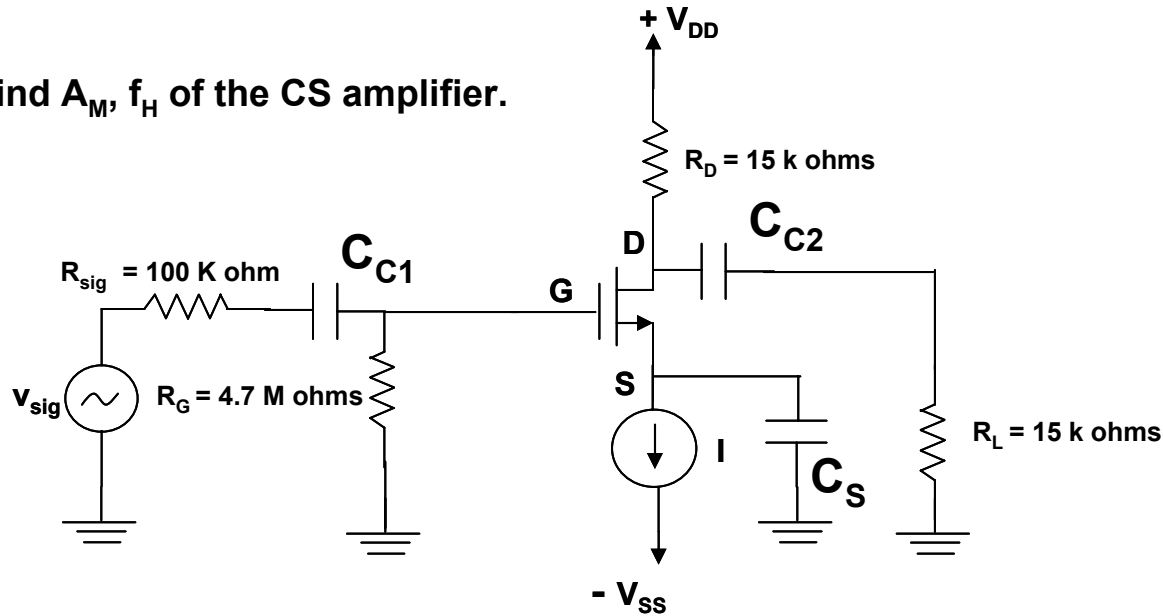
### Example : High Frequency Response

- The circuit is:
- Find  $A_M$ ,  $f_H$  of the CS amplifier.



$C_{gs} = 1 \text{ pF}$   
 $C_{gd} = 0.4 \text{ pF}$   
 $g_m = 1 \text{ mA/V}$   
 $r_o = 150 \text{ k}\Omega$

- **Solution:**

$$A_M = -\left( \frac{R_G}{R_G + R_{sig}} \right) g_m R'_L$$

$$R'_L = r_o \parallel R_D \parallel R_L = 150 \parallel 15 \parallel 15 = 7.14 \text{ k ohms}$$

$$g_m R'_L = 1 \times 7.14 = 7.14 \text{ V/V}$$

$$\text{So } A_m = -7 \text{ V/V}$$


- Now  $C_{eq} = (1 + g_m R'_L) C_{gd} = 3.26 \text{ pF}$
- And  $C_{in} = C_{gs} + C_{eq} = 1 + 3.26 = 4.26 \text{ pF}$
- Finally  $f_H = 1/2\pi C_{in} (R_{sig} \parallel R_G) = 382 \text{ k Hz.}$
- QED?





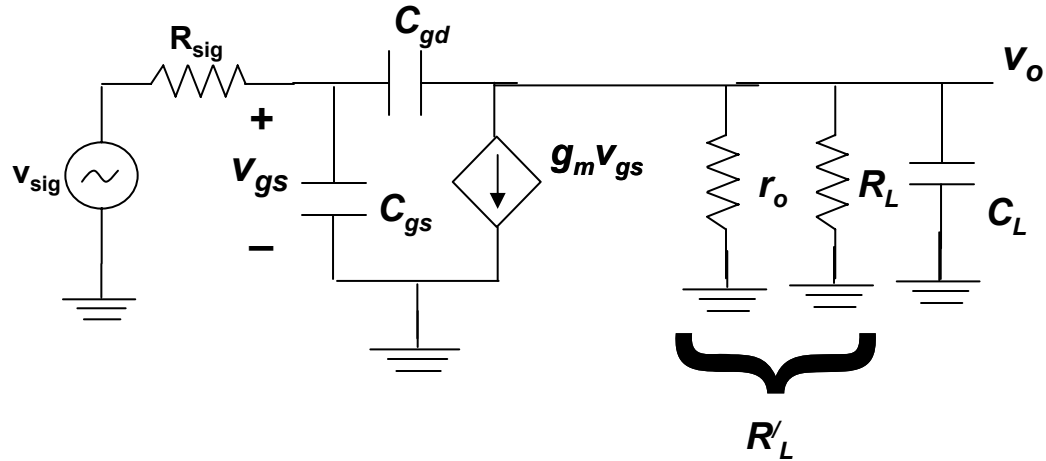
## Active-Loaded Common Source : High Frequency Response

- High-frequency equivalent-circuit model of CS amplifier is:



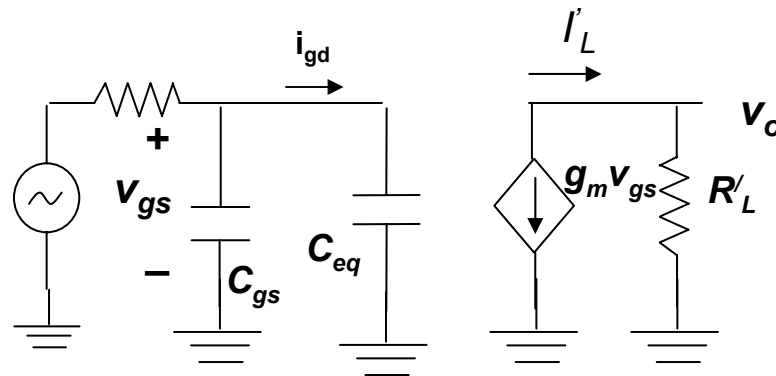And when  $R_{sig}$  is relatively large and  $C_L$  is relatively small,



where  $C_{eq} = (1 + g_m R'_L) C_{gd}$



$$A_M = -g_m R'_L \qquad f_H = \left( \frac{1}{2\pi C_{in} R_{sig}} \right)$$

- QED!


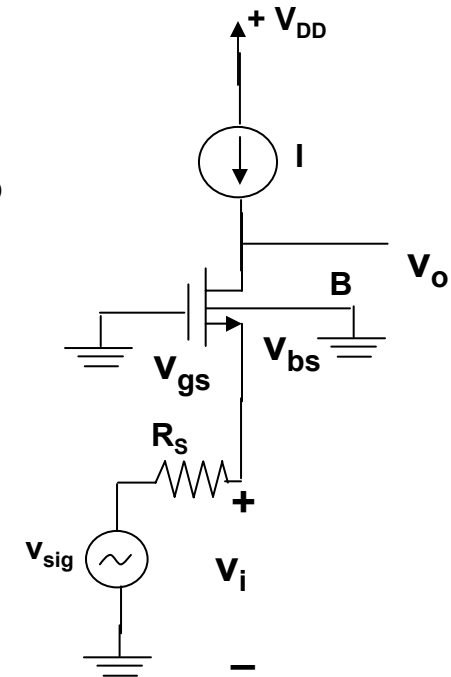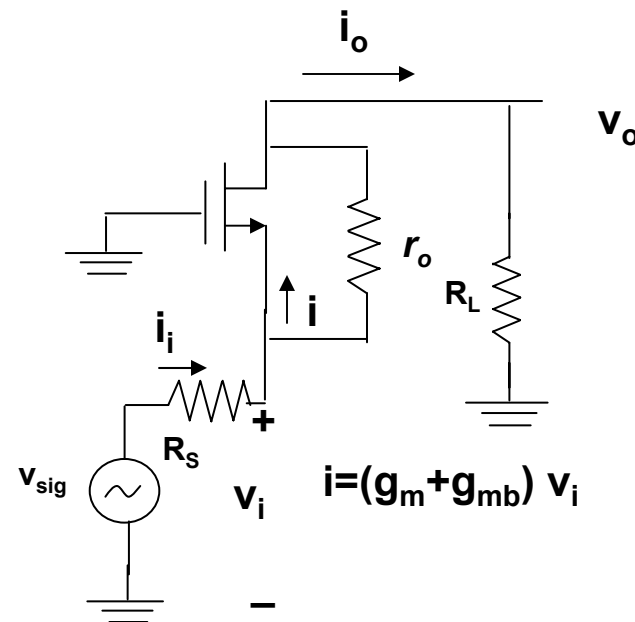
## The CG Amplifier With Active Load

- Consider the following circuit:
- Body transconductance  $g_{mb} = \chi g_m$  where  $\chi = 0.1$  to  $0.2$
- Note  $v_{bs}$  gives rise to a drain current signal  $g_{mb} v_{bs}$
- And since both gate and body are grounded, the two voltages are equal.
- For analysis, consider the following circuit:



- Because  $r_o$  connects output to input node so  $R_{in}$  depends on  $R_L$  and  $R_{out}$  on  $R_s$ .
- ...contd!



## The CG Amplifier With Active Load...contd

11

- Now  $v_o = i_i R_L$
- At source node  $i_i = (g_m + g_{mb}) v_i + i_{ro}$

• Now

$$i_{ro} = \frac{v_i - v_o}{r_o} = \frac{v_i - i_i R_L}{r_o}$$

• So

$$i_i = (g_m + g_{mb}) v_i + \frac{v_i - i_i R_L}{r_o}$$

• Or

$$i_i r_o + i_i R_L = [(g_m + g_{mb}) r_o + 1] v_i$$


• And

$$i_i = \frac{[1 + (g_m + g_{mb}) r_o] v_i}{r_o + R_L}$$

• Finally

$$R_{in} = \frac{v_i}{i_i} = \frac{r_o + R_L}{[1 + (g_m + g_{mb}) r_o]}$$

• ...contd!

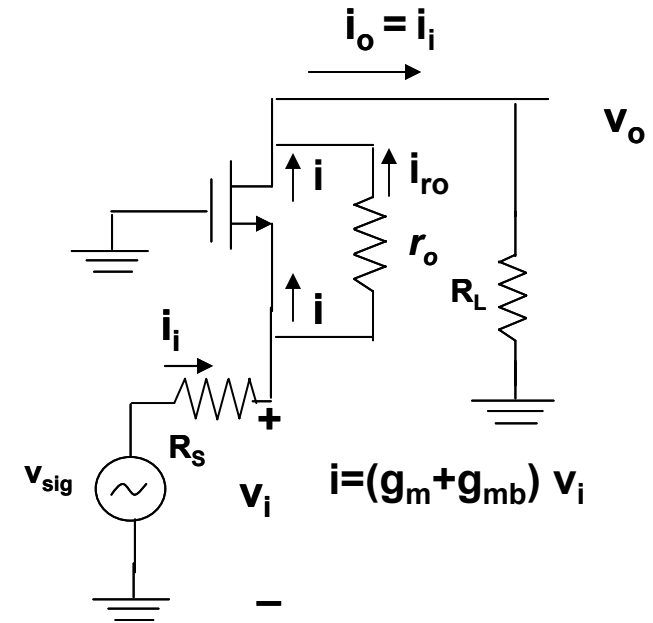

## The CG Amplifier With Active Load...contd

- For voltage gain:  $v_o = i_o R_L = i_i R_L$  and  $v_i = i_i R_{in}$
- So  $A_v = v_o/v_{in} = R_L/R_{in}$
- For  $A_{vo}$ ?
- $i r_o + v_i = v_o$  (because  $R_L = \alpha$  so  $i$  flows from top to bottom)
- And  $i = (g_m + g_{mb})v_i$
- So  $v_o = (g_m + g_{mb})v_i r_o + v_i$
- Or  $A_{vo} = 1 + (g_m + g_{mb})r_o$
- Now

$$R_{in} = \frac{v_i}{i_i} = \frac{r_o + R_L}{[1 + (g_m + g_{mb})r_o]}$$


- Therefore

$$R_{in} = \frac{r_o + R_L}{A_{vo}}$$

- Hence

$$A_v = \frac{R_L}{R_{in}} = A_{vo} \frac{R_L}{r_o + R_L}$$

- ...contd!

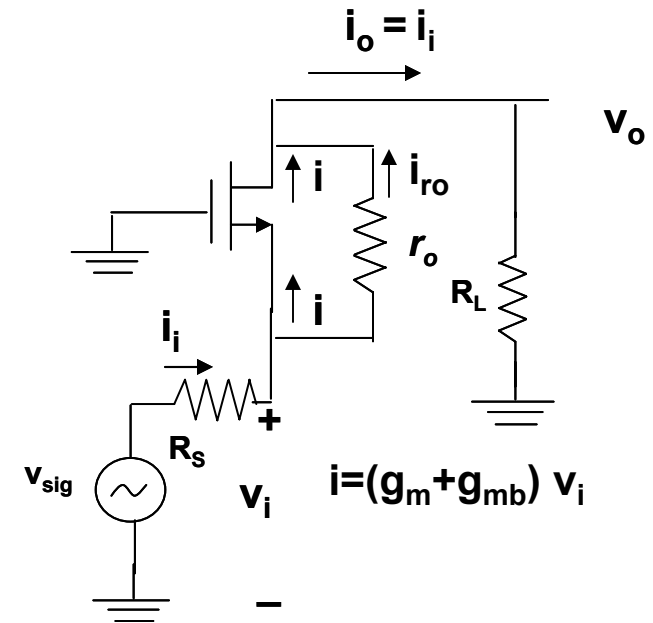

## The CG Amplifier With Active Load...contd

- There are two output resistances:- $R_o$  when  $v_i = 0$  and  $R_{out}$  when  $v_{sig} = 0$ .

- So  $R_o = r_o$


- For  $R_{out}$   $v_x = [i_x + (g_m + g_{mb})v]r_o + v$

- And

$$R_{out} = r_o + [1 + (g_m + g_{mb})r_o]R_s$$

- Finally

$$R_{out} = r_o + A_{vo}R_s$$

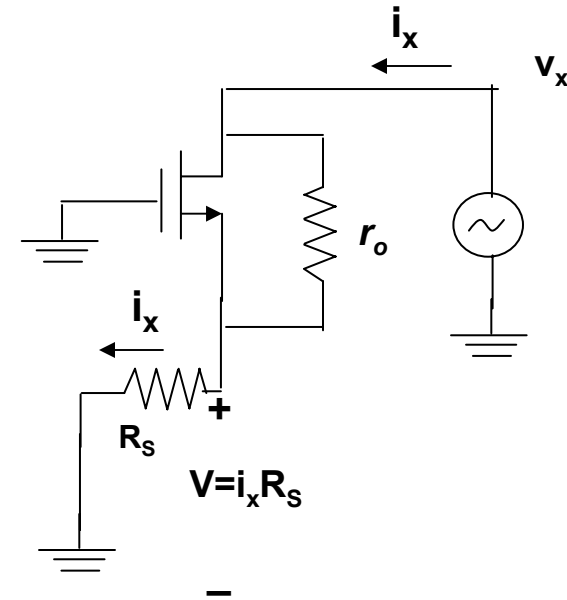

- CB Amplifier with active-load!



## The CB Amplifier With Active Load



- **Similar treatment as CG but with finite  $\beta$ . Additionally, the base conducts signal current contrary to the behaviour of a MOSFET CG amplifier.**
- **Emitter degeneration resistance!**



## The CE Amplifier With Emitter Degeneration Resistance

- Emitter degeneration is more useful in CE amplifier than source degeneration in the CS amplifier.
  - Because emitter degeneration increases the input resistance of the CE amplifier.
  - Incidentally the input resistance of CS is practically infinite to begin with.

- The circuit:

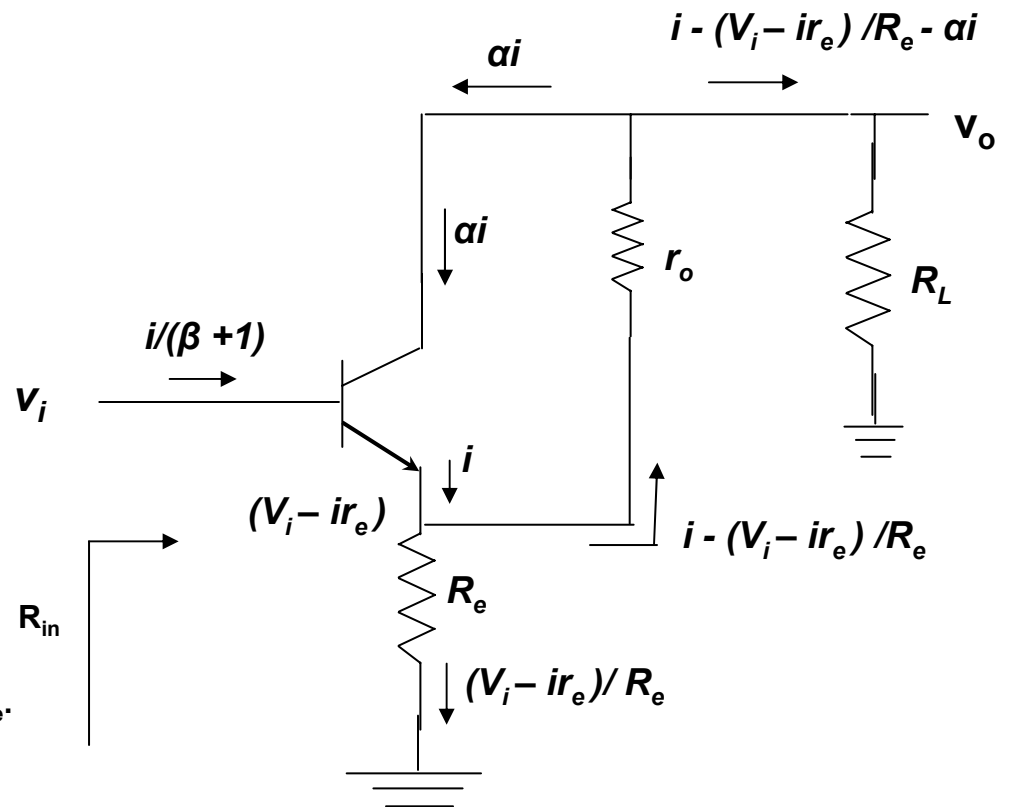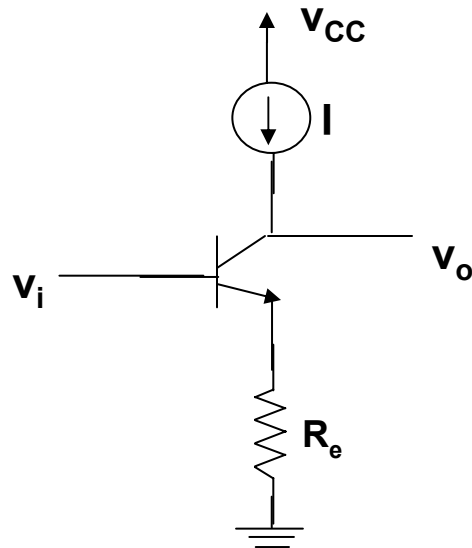

- $R_e$  is usually in the range of 1 to 5 times  $r_e$ .
- The analysis?
- $v_o = (V_i - ir_e) - r_o \{i - (V_i - ir_e) / R_e\}$
- ...contd!



## The CE Amplifier With Emitter Degeneration Resistance...contd

- So  $v_o = (V_i - ir_e) - r_o \{i - (V_i - ir_e)/R_e\}$  and  $v_o = [i - (V_i - ir_e)/R_e - \alpha i]R_L$
- And solving these two equations simultaneously gives us  $R_{in} = V_i/[i/(\beta + 1)]$
- Or:

$$R_{in} = (\beta + 1)r_e + (\beta + 1)R_e \frac{r_o + \frac{R_L}{\beta + 1}}{r_o + R_L + R_e}$$

- Can be simplified to:

$$R_{in} = (\beta + 1)r_e + (\beta + 1)R_e \frac{1}{1 + \frac{R_L}{r_o}}$$

- Hence inclusion of  $R_e$  :
  - Reduces effective transconductance by a factor  $(1 + g_m R_L)$
  - Increases its output resistance by the same factor
  - Increases input resistance depending on the value of  $R_L$ .
  - Increases amplifier bandwidth and finally the emitter degeneration resistance  $R_e$  increases the linearity of the amplifier.
- The CS Amplifier!







## The CS Amplifier With Source Degeneration Resistance

- The source degeneration resistance introduces negative feedback.
  - Broadens the bandwidth.
  - More control over the amplifier.
- 
- The Emitter Follower!


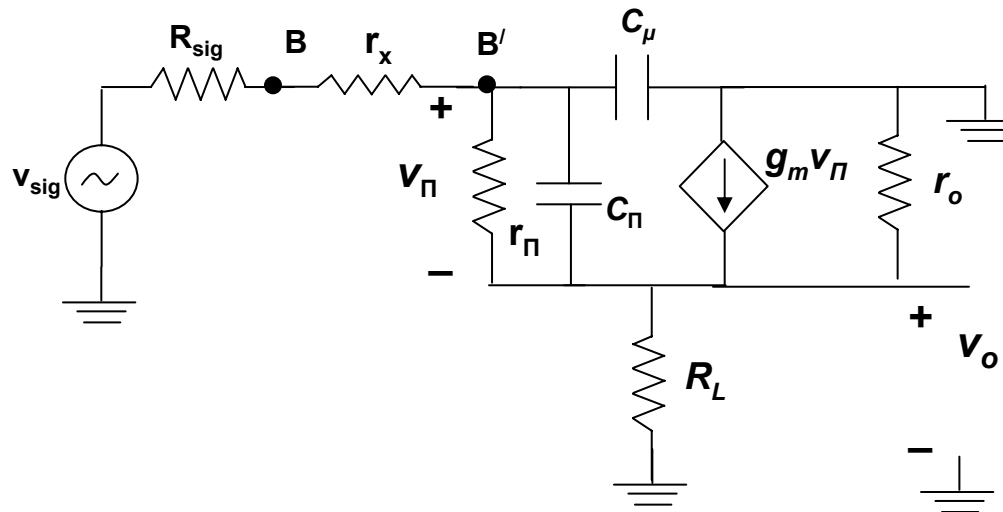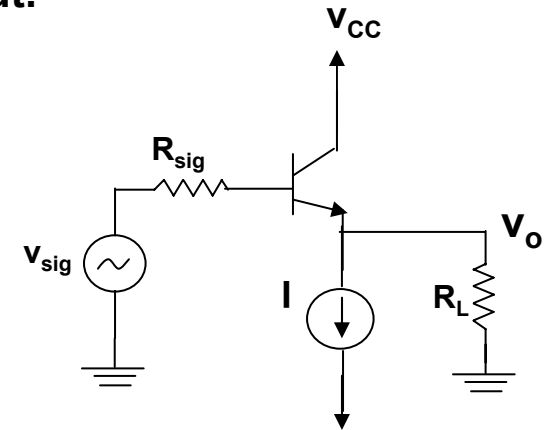
## The Emitter Follower


- The common–collector is also called emitter-follower because the voltage at the emitter follows very closely the voltage at the input.
- The emitter-follower suitable for IC fabrication is:
- Low frequency gain, input resistance and output resistance is identical to capacitively coupled version studied earlier.
- The high-frequency circuit is:




- Simplified circuit!



## The Emitter Follower...contd

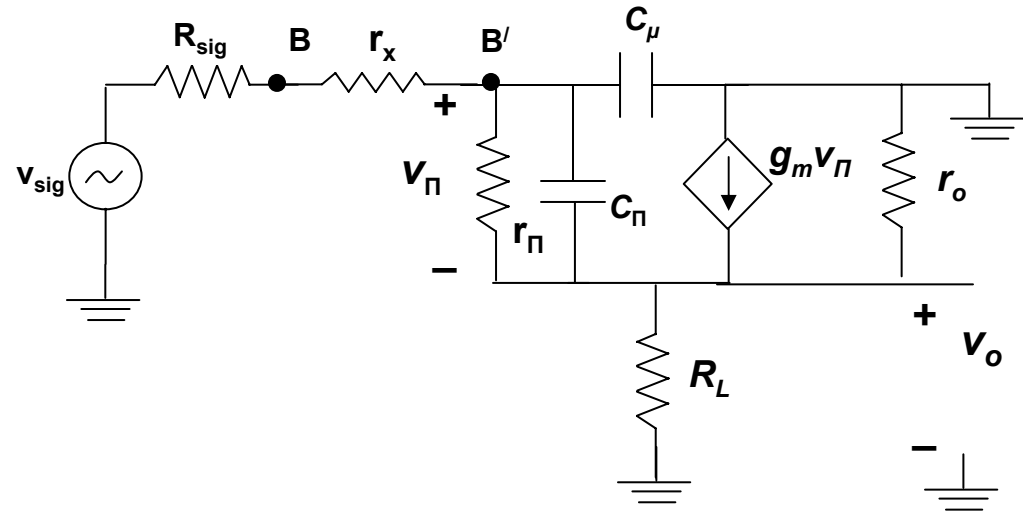

- The simplified circuit is:

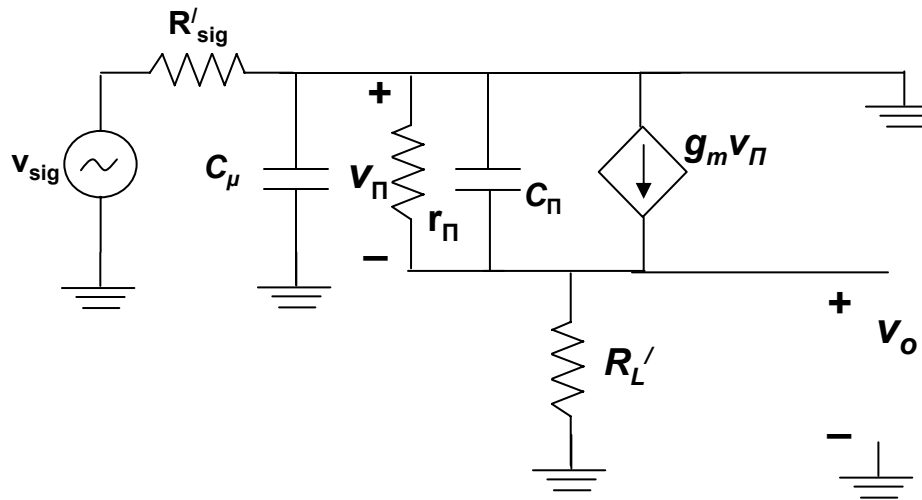

- Here  $R'_{sig} = ?$  and  $R'_L = ?$
- Simplified circuit!



## The Emitter Follower...contd

20

- The simplified circuit is:
- The resistance seen by  $C_\mu$  is the parallel equivalent of  $R'_{sig}$  and input resistance:

$$R_\mu = R'_{sig} \parallel [r_\pi + (\beta + 1)R'_L]$$


- And resistance seen by  $C_\pi$  is:

$$R_\pi = \frac{R'_{sig} + R'_L}{1 + \frac{R'_{sig}}{r_\pi} + \frac{R'_L}{r_e}}$$

- The high-frequency is:

$$f_H = \frac{1}{2\pi(C_\mu R_\mu + C_\pi R_\pi)}$$

- Home Assignment!

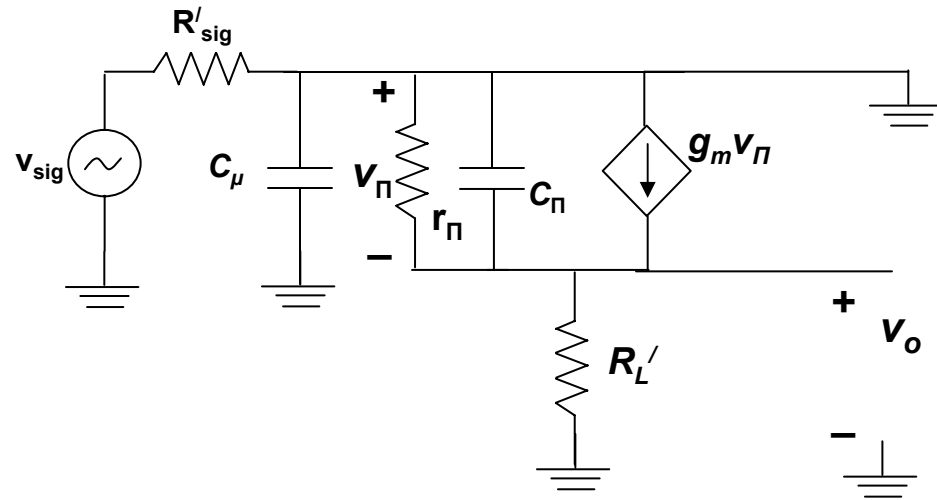

## The Emitter Follower

# Home Assignment

## Ex : 6.35


- ...Some useful transistor pairings!


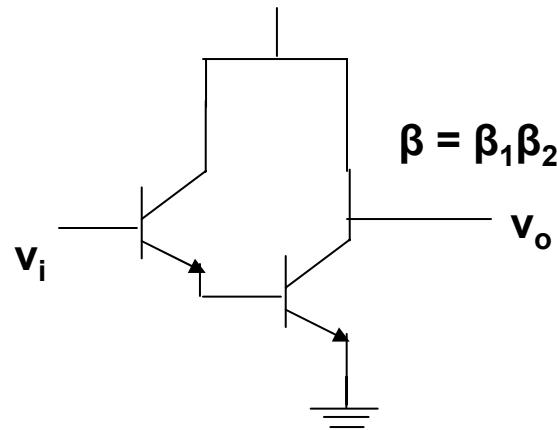
## Some Useful Transistor Pairings

22

- Sometimes the transistor pairings are done in such a way that the superior performance is achieved through maximizing the advantages and minimizing the shortcomings of each of the two individual configurations.
- In such cases the transistor pair is considered as a compound device and the resulting amplifier is considered as a single stage.
- The Darlington Configuration:





- ...contd!


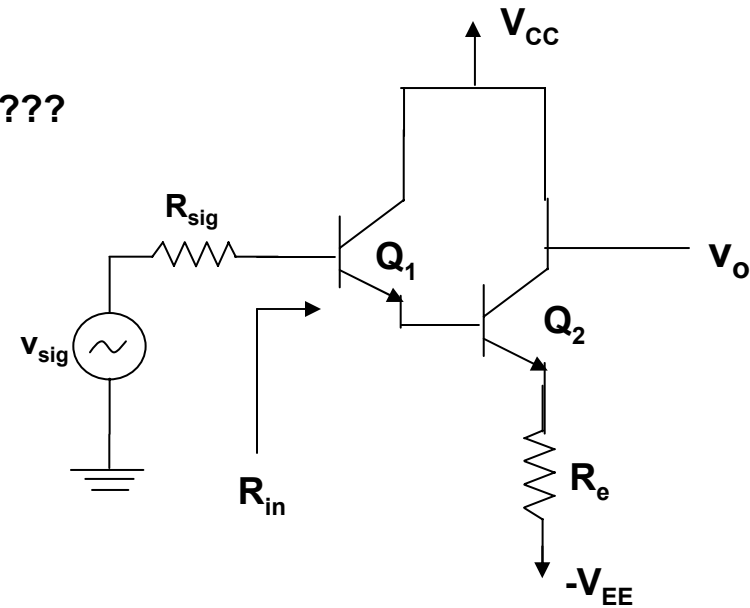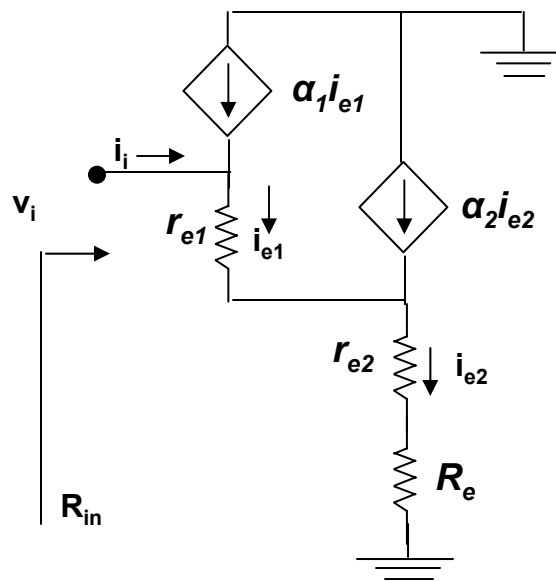
## Example : Transistor Pairings

- Consider the circuit shown. If  $\beta_1=50$ ,  $\beta_2=100$ ,  $R_E=500 \Omega$  and  $r_{e1}=r_{e2}=25 \Omega$  determine the value of  $R_{in}$ .

- Solution:  $R_{in} = (\beta_1 + 1) \{r_{e1} + (\beta_2 + 1) (r_{e2} + R_e)\}$  ????



- QED!



## Single-stage IC Amplifiers : Summary

- IC technology offers the circuit designers a very large number of inexpensive small-area MOS transistors.
- For minimization of chip area, large-valued resistors and capacitors are virtually absent.
- Biasing in integrated circuits utilizes current sources.
  - An accurate and stable reference current is generated and then replicated to provide bias currents for various amplifier stages.
  - The heart of the current-steering circuitry utilized to perform this function is the current-mirror.
- The high-frequency response of IC amplifiers is limited by the transistor internal capacitances, mainly  $C_{gs}$  and  $C_{gd}$  in the MOSFET and  $C_{\pi}$  and  $C_{\mu}$  in the BJT.
- IC amplifiers employ constant-current sources in place of the resistances  $R_D(R_C)$  that connects the drain (collector) to the power supply. Reason?
  - These active loads enable the realization of reasonably large voltage gains while using low voltages supplies (as low as 1 V)

...contd





- The largest voltage gain available from a CS or a CE amplifier is equal to the intrinsic gain of the transistor:  $A_o = g_m r_o$ 
  - for a BJT, it is 2000 to 4000 V/V.
  - for a MOSFET, it is 20 to 100 V/V.
    - CE amplifier has low input resistance and
    - CS amplifier has an infinite input resistance
- Including a small resistance in the source (emitter) of a CS(CE) amplifier provides the designer with a tool to effect some performance improvements e.g. wider bandwidth in return for gain reduction (a trade-off characteristic of negative feedback).
- Note some of the ICs dissipate as much as 100 watts.
- End of the part.



**Choose a job you love,  
and you will not have to work a  
day in your life.  
(Confucius)**