

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

# **Differential & Multistage Amplifiers**



A journey of a thousand miles  
begins with  
a single step.

Lao – tzu *Chinese philosopher*  
(604 BC - 531 BC)

## Differential & Multistage Amplifiers

- **Move to more complex analogue circuits and systems.**
- **Differential Amplifiers**
  - **Most widely used building block**
  - **Input stage of every op-amp**
- **These are well-suited for IC fabrication because:**
  - **Performance depends on matching the two sides of the pair**
  - **These utilize more components than single-ended circuits and are economical in IC fabrication**
- **Why differential amplifiers?**
  - **Less sensitive to noise and interference**
    - **If there is interference on the two input wires, the difference only is sensed (interference cancels out)**
  - **Direct coupling is possible thus large capacitances can be avoided**
  - **So ideally suited for IC fabrication because large capacitors are difficult to fabricate economically in IC process**
- **...contd!**



# Difference / Differential Amplifiers

- **What is a difference amplifier?**
  - A difference amplifier is one that responds to the difference between the two signals applied at its inputs.
    - It ideally rejects signals that are common to both inputs.
- **Consider the input signals as  $v_1$  and  $v_2$  :**
  - The difference / differential input signal is:
$$v_{ld} = v_2 - v_1$$
  - The common-mode input signal is the average of the two input signals:
$$v_{lcm} = (v_2 + v_1)/2$$
- **By adding and subtracting to get  $v_1$  and  $v_2$  :**
  - $v_1 = v_{lcm} - (v_{ld})/2$  and
  - $v_2 = v_{lcm} + (v_{ld})/2$
- **Pictorially!**
- **Example : Determine the differential and common-mode input signals when the two inputs are  $v_1 = 1.002$  V and  $v_2 = 0.998$  V.**
- **Solution:  $v_{lcm} = 1$  V and  $v_{ld} = -4$  mV**
- **Output of a Difference/Differential Amplifier!**



## Output of a Difference Amplifier

- Ideally the difference amplifier will amplify only the differential input signal  $v_{ld}$ .
- It will completely reject common-mode input signal  $v_{lcm}$ .
- However, non ideal or practical circuits will have an output voltage :

$$v_o = A_d v_{ld} + A_{cm} v_{lcm}$$

where  $A_d$  denotes amplifier differential gain and  $A_{cm}$  denotes common-mode gain

- A parameter that determines efficacy of a differential amplifier is defined as Common-Mode Rejection Ratio:


$$CMRR = 20 \log \{A_d / A_{cm}\}$$

- Ideally CMRR is infinite because  $A_{cm} = 0$
- Where does the common-mode signal come from?
- The MOS Differential Pair!


 
## The MOS Differential Pair

- The circuit for basic MOS differential pair is :
- Two matched MOS transistors  $Q_1$  and  $Q_2$  with sources joined together by a constant current source  $I$ .
- Operation is such that MOSFET does not enter in triode region of operation.
- Generally active loads are employed instead of  $R_D$ .
- Various modes of operation are possible:
  - Operation with a common-mode input voltage
  - Operation with a differential input voltage
  - Large signal operation
  - Small-signal operation



- Operation with a common-mode input voltage!



## Operation with a Common – Mode Input Voltage

- The circuit:
- The two gates are joined together and connected to a voltage  $v_{cm}$  called the common-mode voltage
- So  $V_{G1} = V_{G2} = V_{CM}$
- And  $V_S = V_{CM} - V_{GS}$
- Since  $Q_1$  &  $Q_2$  are matched  $i_{D1} = i_{D2} = I/2$
- $V_{GS}$  is gate to source voltage corresponding to a drain current of  $I/2$


- Neglecting channel length modulation, the  $v_{CM}$  drain current is:

$$I_{D1} = I_{D2} = \frac{I}{2} = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

- Or:
- $$\frac{I}{2} = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_{GS} - V_t)^2 = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_{ov})^2$$

- And:
- $$V_{ov} = \sqrt{\frac{I}{k'_n \left( \frac{W}{L} \right)}}$$

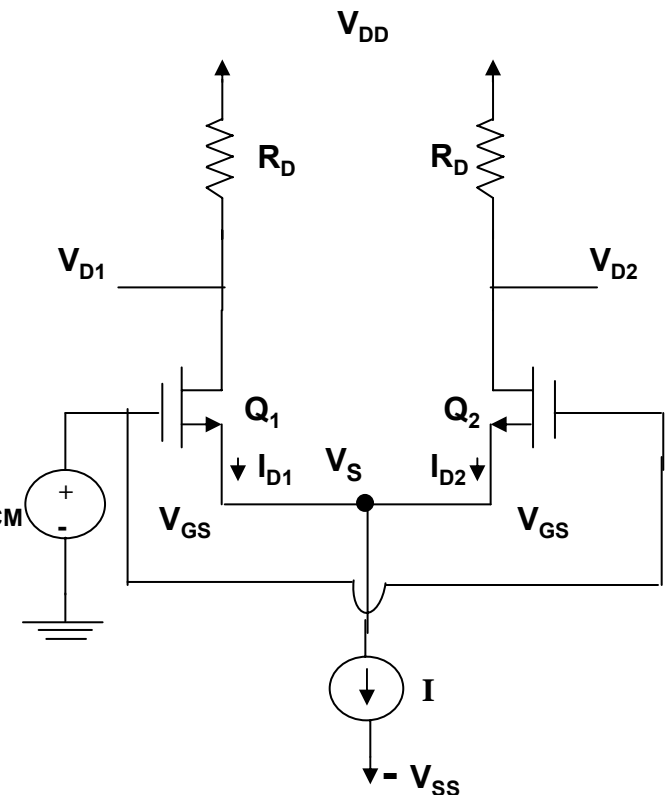- Operation with a common-mode input voltage...contd!






## Operation with a Common – Mode Input Voltage...contd

- The voltage at each drain:

$$V_{D1} = V_{D2} = V_{DD} - I/2R_D$$

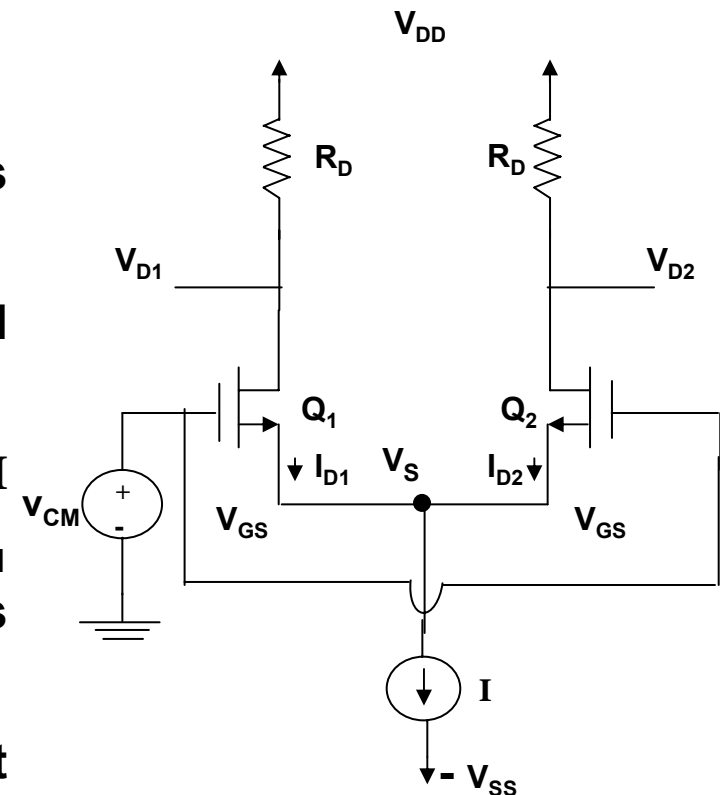- The difference in voltage of two drains is zero.
- The differential pair does not respond to (it rejects) common-mode i/p signals.
- Varying the value of  $v_{cm}$ , current  $I$  continues to divide equally between  $Q_1$  and  $Q_2$  as long as the transistors remain in saturation.
- The voltages at the drain will not change.




- Operation with a differential input voltage!


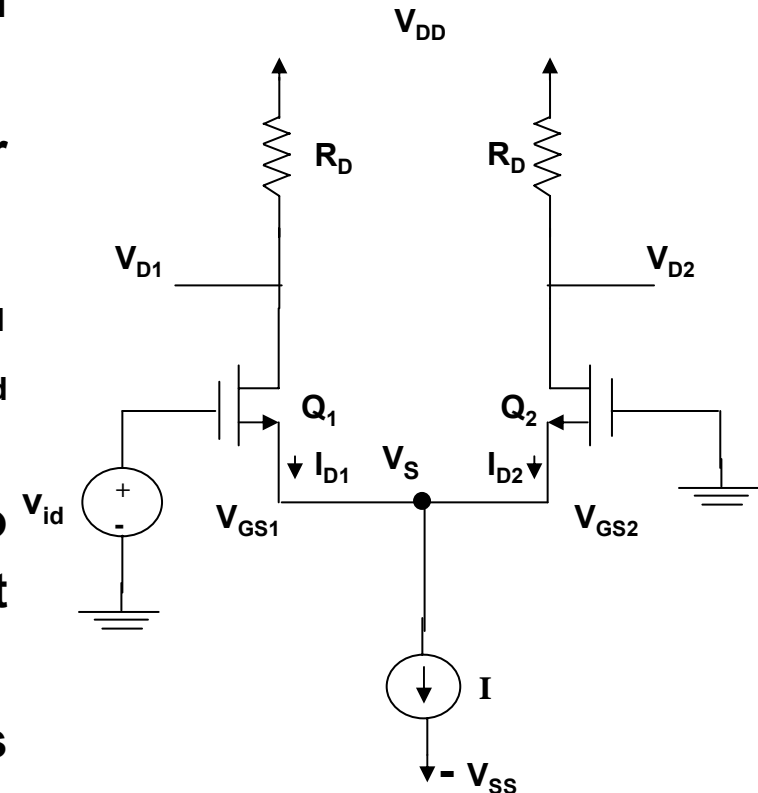
## Operation with a Differential Input Voltage

- The circuit:
- We apply a difference or differential input voltage:  $V_{id} = V_{GS1} - V_{GS2}$
- If  $V_{id}$  is positive,  $V_{GS1}$  will be greater than  $V_{GS2}$  and hence  $i_{D1} > i_{D2}$
- The difference output voltage  $V_{D2} - V_{D1}$  will be positive and vice versa when  $V_{id}$  is negative.
- So the differential pair responds to difference-mode or differential input signals.
- At some value of  $v_{id}$ , the entire bias current will flow in one of the two transistors.



- For example; when  $v_{GS1}$  reaches the value that corresponds to:

$$i_{D1} = I = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_{GS1} - V_t)^2$$

- ...contd!



## Operation with a Differential Input Voltage...contd

11

$$i_{D1} = I = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (V_{GS1} - V_t)^2$$


- So:

$$V_{GS1} = V_t + \sqrt{\frac{2I}{k'_n \left( \frac{W}{L} \right)}}$$

- Or:

$$V_{GS1} = V_t + \sqrt{2} V_{ov}$$

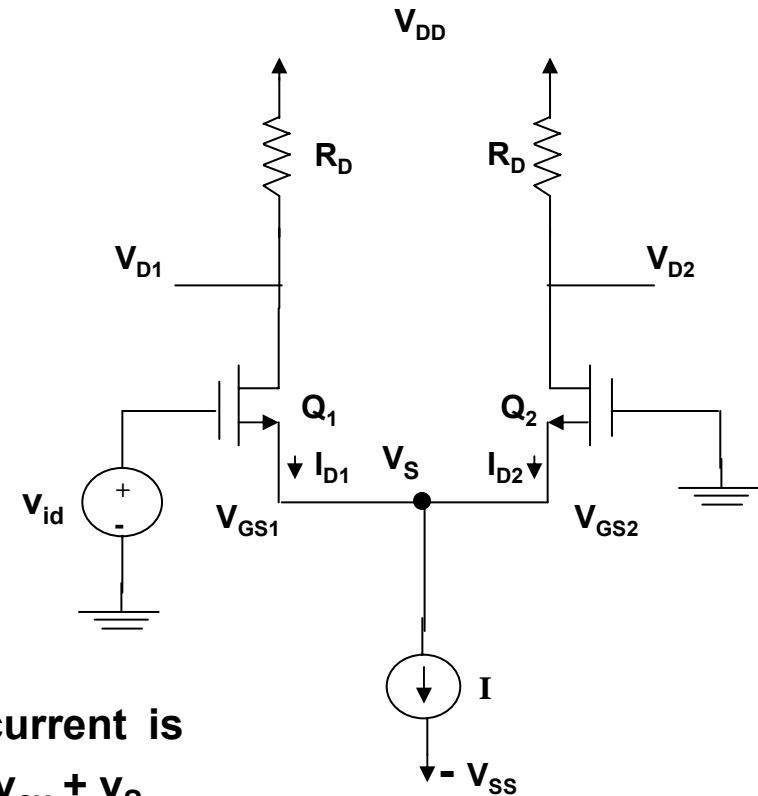where  $v_{ov}$  is the overdrive voltage corresponding to a drain current of  $I/2$ .



- The value of  $v_{id}$  at which the entire bias current is steered into  $Q_1$  is  $v_{idmax} = V_{GS1} + V_S = v_t + \sqrt{2} v_{ov} + V_S$
- Now  $v_s = -v_t$  for cutting off  $Q_2$ .
- Hence  $v_{idmax} = \sqrt{2} v_{ov}$
- And in the negative direction  $v_{idmax} = -\sqrt{2} v_{ov}$
- Therefore the range is?
- Differential Amplifier as a linear amplifier!



## Operation as a Linear Amplifier

- Use of differential amplifier as a linear amplifier?
- Keep input signal small.
- This small signal increases current in one transistor and decreases proportional current in the other transistor by an amount  $\Delta I$ .
- So current becomes  $I/2 + \Delta I$  and  $I/2 - \Delta I$
- A voltage signal  $-\Delta I R_D$  and  $+\Delta I R_D$  develops at the other transistor.
- The output voltage taken between the two drains will be  $2 \Delta I R_D$  which is proportional to differential input signal  $v_{id}$ .
- Large –signal operation!

